



1 (20pt)	2 (20 pt)	3 (20 pt)	4 (20 pt)	5 (20 pt)	Total (100 pt)

1. Show the systematic sequence of transformations when we solve a problem using a computer


Sequence	Explanation	An example

2. Write the Two's complement representation of the decimal numbers given in the table

Decimal Number	Two's complement (1 sign bit + 7bits)
+21	
-21	
+57	
-15	

3. By using the formula below, write the floating point number corresponding to


Binary representation	Floating Point Value
10000101011000000000000000000000	

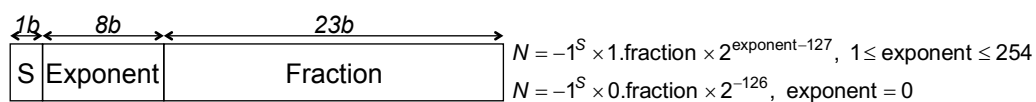




4. For the transistor-level circuit in the figure below, fill in the truth table. What is Z in terms of A and B?

A	B	C	D	Z

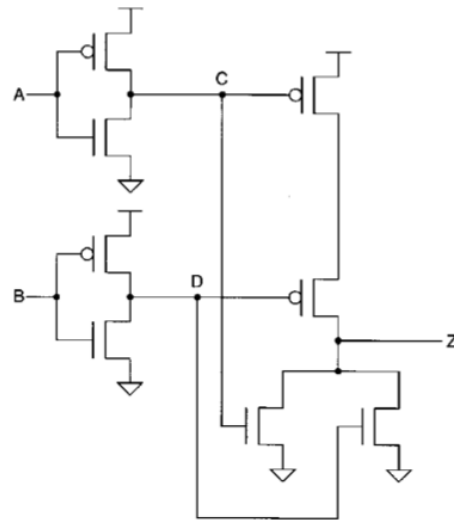

5. Given the logic circuit below, fill in the truth table for the output value Z.

A	B	C	Z
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

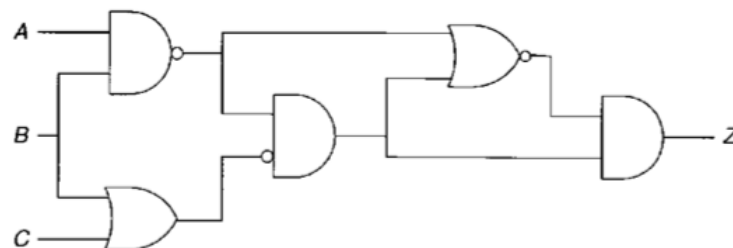



1 (20pt)	2 (20 pt)	3 (20 pt)	4 (20 pt)	5 (20 pt)	Total (100 pt)

1. Show the systematic sequence of transformations when we solve a problem using a computer


Sequence	Explanation	An example

2. Write the Two's complement representation of the decimal numbers given in the table

Decimal Number	Two's complement (1 sign bit + 7bits)
+21	
-21	
+57	
-15	

3. By using the formula below, write the floating point number corresponding to


Binary representation	Floating Point Value
10000101011000000000000000000000	

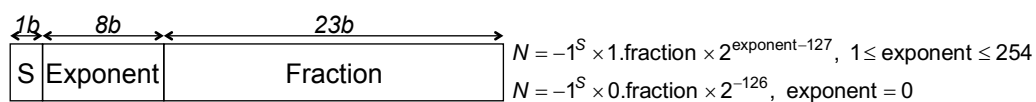




4. For the transistor-level circuit in the figure below, fill in the truth table. What is Z in terms of A and B?

A	B	C	D	Z

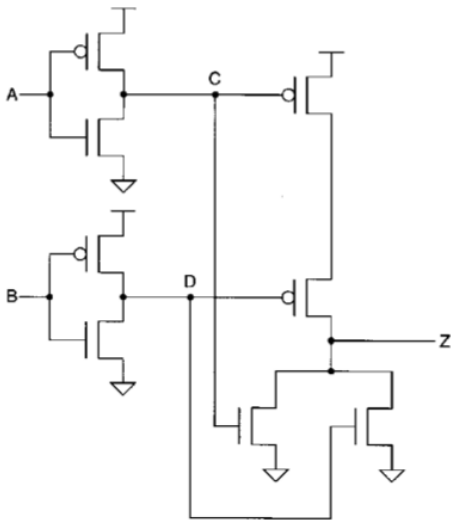

5. Given the logic circuit below, fill in the truth table for the output value Z.

A	B	C	Z
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

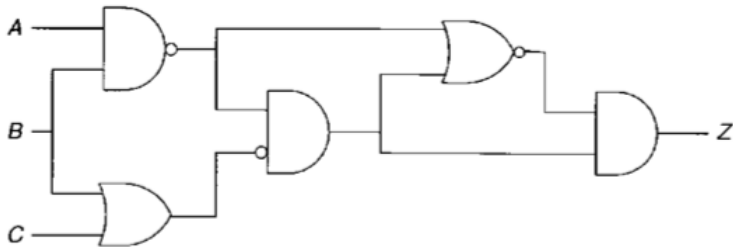



1 (20pt)	2 (20 pt)	3 (20 pt)	4 (20 pt)	5 (20 pt)	Total (100 pt)

1. Show the systematic sequence of transformations when we solve a problem using a computer


Sequence	Explanation	An example

2. Write the Two's complement representation of the decimal numbers given in the table

Decimal Number	Two's complement (1 sign bit + 7bits)
+21	
-21	
+57	
-15	

3. By using the formula below, write the floating point number corresponding to


Binary representation	Floating Point Value
10000101011000000000000000000000	

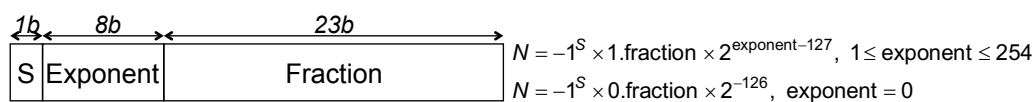



4. For the transistor-level circuit in the figure below, fill in the truth table. What is Z in terms of A and B?

A	B	C	D	Z

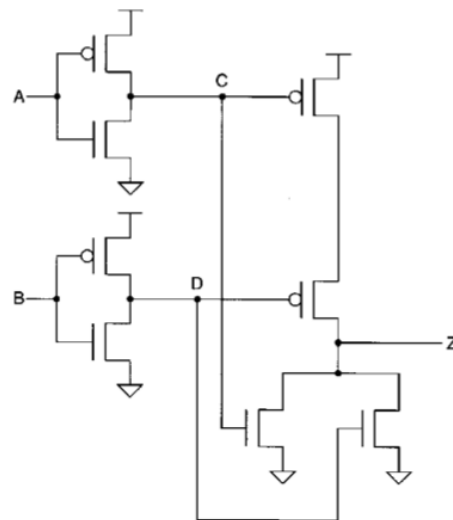

5. Given the logic circuit below, fill in the truth table for the output value Z.

A	B	C	Z
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

